

# 1 VHDL

Every VHDL structure must have an entity, which describes the appearance of the device externally, and an architecture that defines the way it implements the entity.

All connections are PORTs, which must be uniquely named in the entity definition. They can have a mode (IN, OUT, INOUT, BUFFER) a type (BIT, BIT\_VECTOR) and a set of levels (BIT\_VECTOR (0 TO 3)).

Variables are known as SIGNALs, which have the same properties as PORTs.

The entity

```

ENTITY logic IS PORT
(
    a,b,c: IN BIT;
    f: OUT BIT);
END logic;

ARCHITECTURE archlogic OF logic IS
    SIGNAL d:BIT
BEGIN
    d <= a AND b;
    g : nor2 PORT MAP (c,d,f);
END archlogic;

```